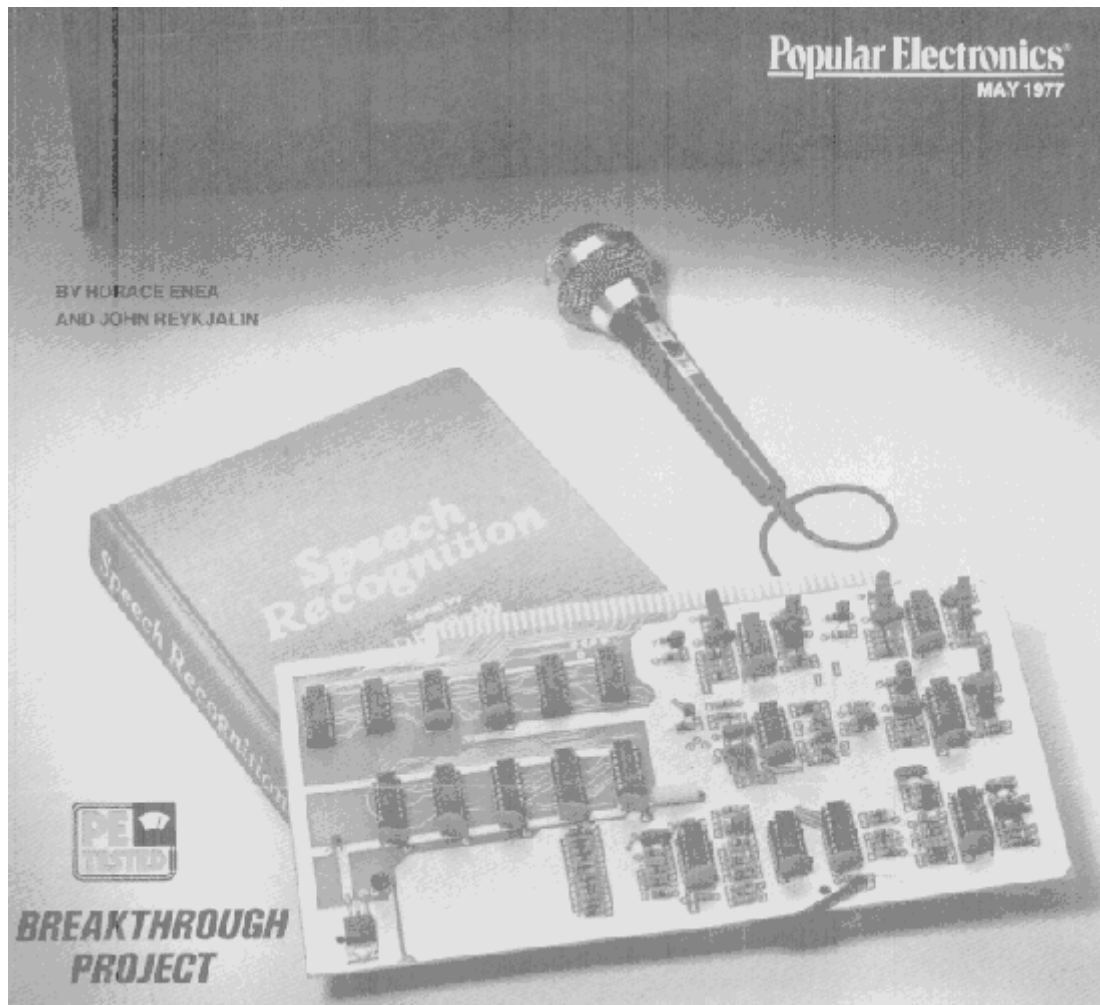


sp recog Speech Lab

Speechlab

dropbox



INTRODUCING SPEECHLAB - THE FIRST HOBBYIST VOCAL INTERFACE FOR A COMPUTER!

Now your computer can respond to vocal commands by the simple addition of a \$250 single-board unit.

IMAGINE being able to talk to your computer and have it respond by way of a hard-copy device or by activating some external appliance! Computer hobbyists can now enjoy this facility by building "Speechlab", a new, low-cost (under \$250) computer peripheral. To use it, all one does is plug the single Speechlab PC board into an Aftair-bus connector (used by many microcomputer manufacturers), enter a special program, and the computer does the rest. It's a state-of-the-art approach at a moderate cost. One section of the program allows the user to "train" the computer to accept a vocal input (via a microphone), analyze the spoken word, and create a digitized version that is stored in memory. The second part of the program allows the user to speak to the Speechlab and have the computer generate the output selected for that particular sound. The vocabulary size of Speechlab is a function of the

speech recognition algorithm used and the amount of memory available. For the program used in this article, it is 64 bytes per spoken word. The unique characteristics of Speechlab open many formerly closed doors. Since Speechlab will operate with any audio input (not necessarily a recognized language), a person who's vocally handicapped can operate almost any number of appliances (TV receiver, stereo system, solenoid-operated door, etc.) using a repeatable sound such as a grunt. One can use Speechlab, too, as a vocal processor to add spoken commands to many computer games (such as the "Star Trek" game), or enter the world of artificial intelligence and advanced programming.

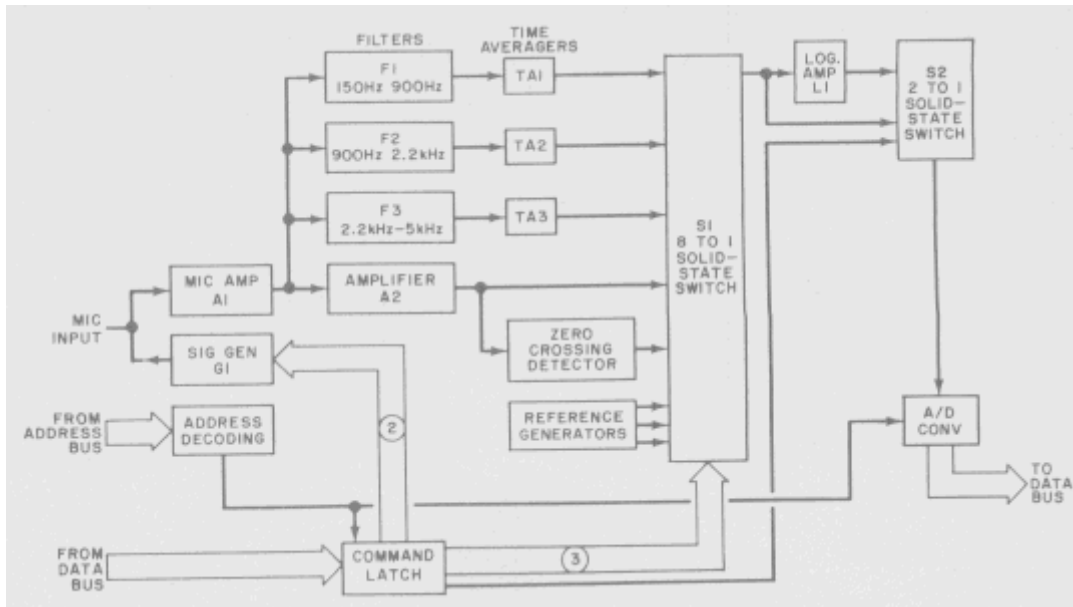


fig. 1. The mic input is amplified, filtered and applied to S1 along with raw audio, zero-crossing detection, and three reference voltages. Output of S1 is computer selected by switch S2 for digitizing.

Circuit Operation.

The basic block diagram of Speechlab is shown in **Fig. 1**. The audio input is amplified by A1 and applied to three 80-db/decade rolloff band-pass filters F1, F2, and F3. These filters encompass the ranges of 150 to 900 Hz, 900 Hz to 2.2 kHz, and 2.2 kHz to 5 kHz, respectively. These ranges correspond to the frequency ranges of the first three resonances of the average human vocal tract.

Each filter is passed to a time averager (TA1, T2, and TA3) to generate a voltage proportional to the level of the speech waveform within each band. The amplified audio signal from A1 is further amplified by A2 to generate an unfiltered waveform that can swing approx. 2 volts about a rest level of 2 volts. This signal is also applied to a zero-crossing detector that generates a voltage proportional to the number of times the speech waveform crosses the 2-volt rest level in a given period of time, thus generating a measure of the dominant frequency in the speech signal.

These five voltages TA1, TA2, TA3, A2, and ZCD are fed to solid-state switch S1 along with three reference voltages used for calibration and self test. A computer output command selects one of these five voltages to be passed through S1.

The selected output from S1 is passed to a second solid-state switch (S2), and to a logarithmic amplifier (L1) that emphasizes the low-level signal before being passed to S2. Switch S2 can select either the direct output from S1, or the output from L1, and pass this selected signal to a 6-bit A/D converter

where the voltage is converted to a digital value. The output of the A/D converter is fed to the computer data bus.

All operations of the Speechlab are controlled through a single I/O port (address AFhex). As shown in **Fig. 2.**, six bits are used: bit-5 disables the 8-to-1 multiplexer (S1), and is used when switching between bands; bit-4 controls signal generator G1 which is used either to drive the microphone so that it acts like a miniature loudspeaker for prompting during voice input, or to drive the filters and zero-crossing detector during calibration and test; bit-3 selects either linear or logarithmic scaling of the voltage applied to the A/D converter; while bit-2, bit-1, and bit-0 select one of the eight signals from S1 for A/D conversion.

The input data word contains the 6-bit A/D output in bits 0 through 5, bit-6 is unused and is always 0, while bit-7 is the A/D converter status with a 1 corresponding to busy, and 0 corresponding to finished. Speechlab is physically configured to occupy one slot in the Altair bus, and the complete schematic is shown in **Fig. 3. through Fig. 7.**

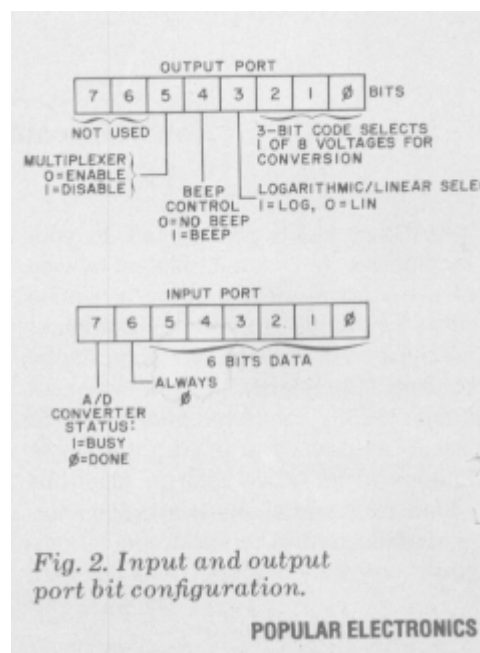


Fig. 2. Input and output port bit configuration.

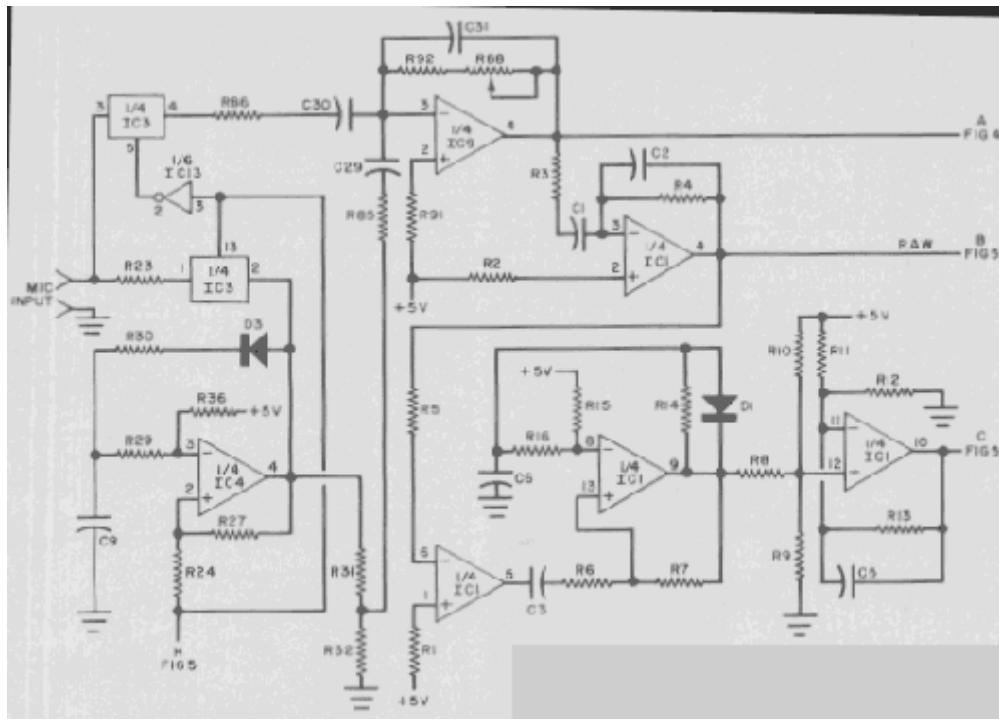


Fig. 3. Amplifier 1/4IC9 takes either audio or tone from 1/4IC4 depending on computer command. IC1 circuits are used as raw amplifier and zero-crossing detector.

PARTS LIST

Unless otherwise noted, the following capacitors are 10% Mylar types, and all picofarad sizes are CMOS types.

C1, C16, C21, C43, C47, C49, C52, C57—0.0047 μ F
 C2, C31—100 pF
 C3, C17, C20—270 pF
 C4, C7, C8, C10, C12, C19, C27, C32, C33, C34, C35, C36, C37, C44, C55, C61, C62—0.1 μ F, 25-V disc
 C5, C14, C18, C24, C54, C60—0.01 μ F
 C6, C42, C45, C53, C56—240 pF
 C9, C40, C48—0.022 μ F
 C11, C29—47 pF
 C13—15 μ F, 25 V tantalum
 C15, C22, C51, C59—0.0015 μ F
 C23—0.0022 μ F
 C25, C26, C28, C38—1 μ F
 C30, C39, C46—0.047 μ F
 C41—0.1 μ F
 C50, C58—0.001 μ F
 D1, D3 through D6—1N4148 or 1N914 diode
 D2—1N746 diode
 IC1, IC4, IC7, IC8, IC9, IC15, IC16—LM5900 quad amp
 IC2—4051 8-to-1 analog multiplex
 IC3—4016 quad analog switch
 IC5—LM311 comparator
 IC6—78M05 5-volt regulator
 IC10—4024 7-stage binary counter
 IC11, IC18—74C174 D flip-flop
 IC12—4050 hex buffer
 IC13, IC22—4049 hex buffer inverter
 IC14—4013 (see text) dual-D flip-flop
 IC17—74LS30 8-input NAND gate
 IC19—8097 three-state hex buffer
 IC20—8093 three-state quad buffer
 IC21—4001 NOR gate
 MIC—Mura DX-121 dynamic microphone (part of stereo set Mura DX-242)

L1—22- μ H choke
 Unless otherwise noted, the following resistors are 1/4-W, 5%

R1—619,000 ohms, 1%
 R2—1 megohm, 1%
 R3—6810 ohms, 1%
 R4—332,000 ohms, 1%
 R5—200,000 ohms, 1%
 R6, R20, R21—30,000 ohms
 R7, R100—3 megohms
 R8, R9, R10, R12, R14, R16, R104—1 megohm
 R11—910,000 ohms
 R13—2.7 megohms
 R15, R48—10 megohms
 R17, R18—20,000 ohms
 R19, R22, R106—10,000 ohms
 R23—1000 ohms
 R24, R27—1.2 megohms
 R25, R34, R39—470,000 ohms
 R26, R38—750,000 ohms
 R28, R31—100,000 ohms
 R29—110,000 ohms
 R30—39,000 ohms
 R32—47,000 ohms
 R33, R41—68,100 ohms, 1%
 R35, R96, R102—75,000 ohms
 R36—3.9 megohms
 R37, R46—357,000 ohms, 1%
 R40, R50, R52, R54, R56, R58, R60
 R61—10,000 ohms, 1%
 R42—12,100 ohms, 1%
 R43, R49—4750 ohms, 1%
 R44—4320 ohms, 1%
 R45, R47—681,000 ohms, 1%
 R51, R53, R55, R57, R59—4990 ohms, 1%
 R62—274,000 ohms, 1%
 R63—7500 ohms
 R64, R66, R72, R75—160,000 ohms
 R65, R71—12,000 ohms

R67, R70—300,000 ohms
 R68—931,000 ohms, 1%
 R69—2 megohms
 R73—620,000 ohms
 R74, R76, R90, R92—62,000 ohms
 R77—15,000 ohms
 R78, R83, R84—147,000 ohms, 1%
 R79, R80, R87—51,100 ohms, 1%
 R81, R82, R89—174,000 ohms, 1%
 R85—330,000 ohms
 R86—680 ohms
 R88—100,000-ohm pc trimmer potentiometer
 R91—270,000 ohms
 R93—249,000 ohms, 1%
 R94—4300 ohms
 R95, R97, R103, R105—360,000 ohms
 R98, R101—820,000 ohms
 R99—845,000 ohms, 1%
 R107—158,000 ohms, 1%
 R108—4700 ohms
 R109, R111, R117, R119—82,000 ohms
 R110, R116—5100 ohms
 R112, R115—180,000 ohms
 R113—549,000 ohms, 1%
 R114—1.6 megohms
 R118—510,000 ohms
 R120—6800 ohms
 R121—2000 ohms

Misc.—Sockets (one 8-pin, thirteen 14-pin, seven 16-pin), regulator mounting hardware, tie-wrap etc.

Note 1: The following is available from Heuristics Inc., 900 N. San Antonio Rd. (Suite C-1), Los Altos CA 94022 (Tele: 415-948-2542): complete kit of all parts including pc board, sockets, microphone, hardware manual, and 200-page lab manual, SpeechBasic, and assembly language programs at \$249. (California residents please add 6 1/4% sales tax.)

Parts list.

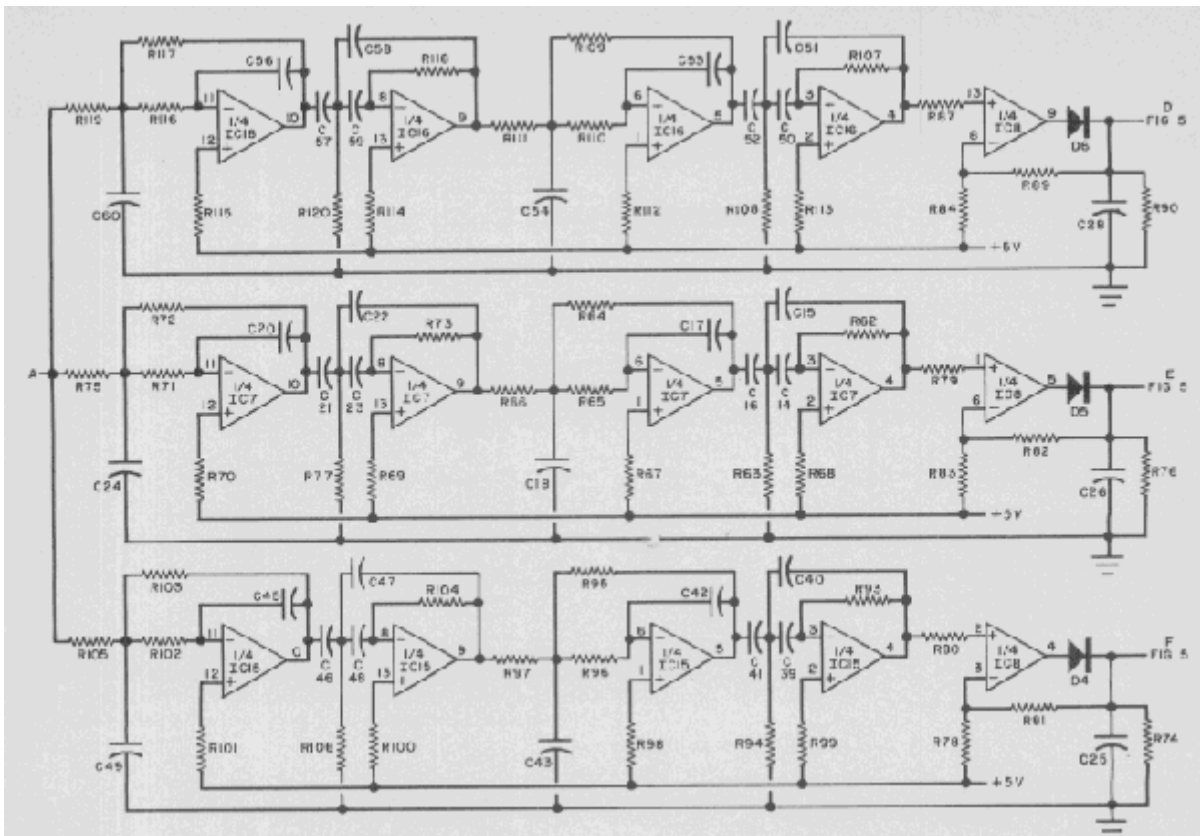


Fig. 4. Three bandpass filters and their associated time averagers. The encompass three ranges corresponding to frequency ranges of the first three resonances of an average human vocal tract.

Construction.

The two foil patterns (Speechlab uses one double-sided PC board) are shown half-size in **Fig. 8**. (Blow up to full size on film only.) Component layout is shown in **Fig. 9**.

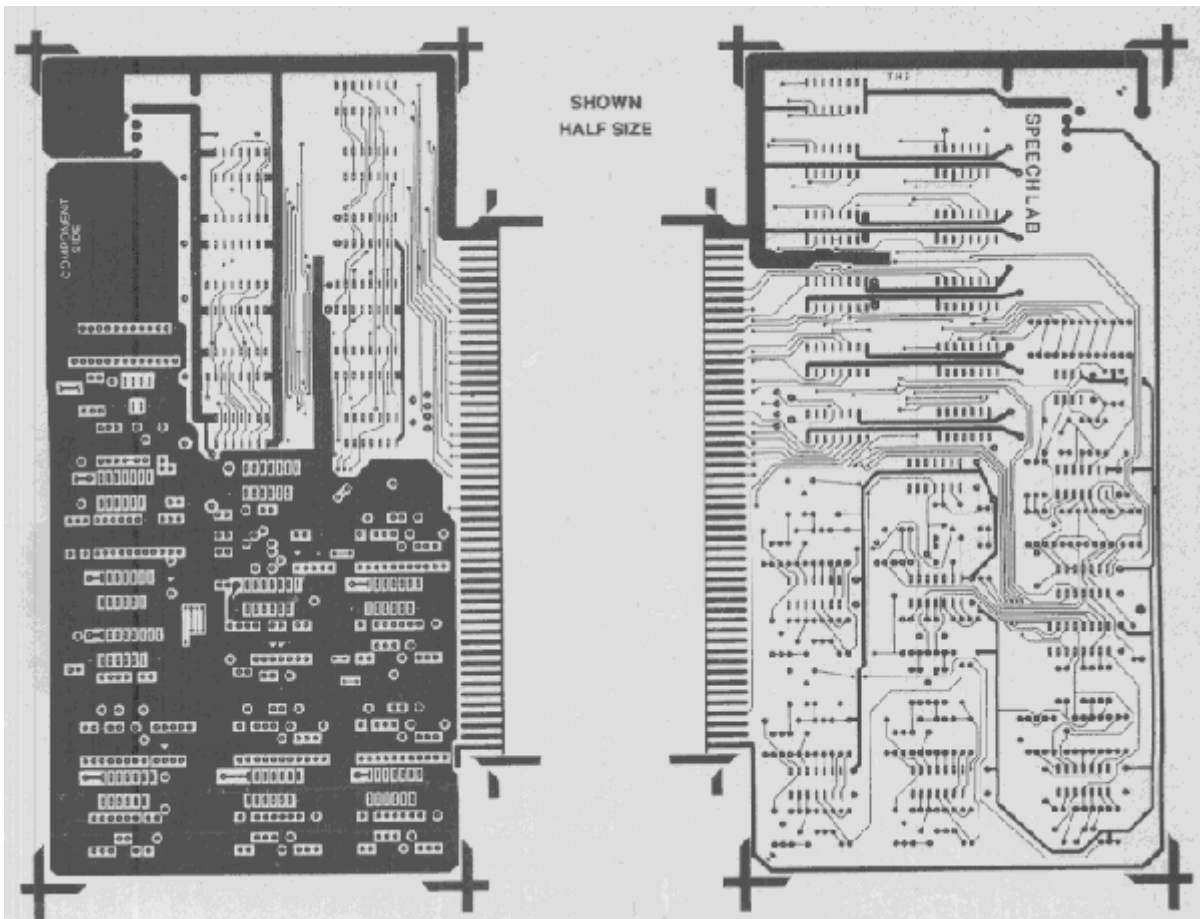


Fig. 8. Etching and drilling guides for pc board are shown half size. Guide at left is the component side. Component layout is in Fig. 9.

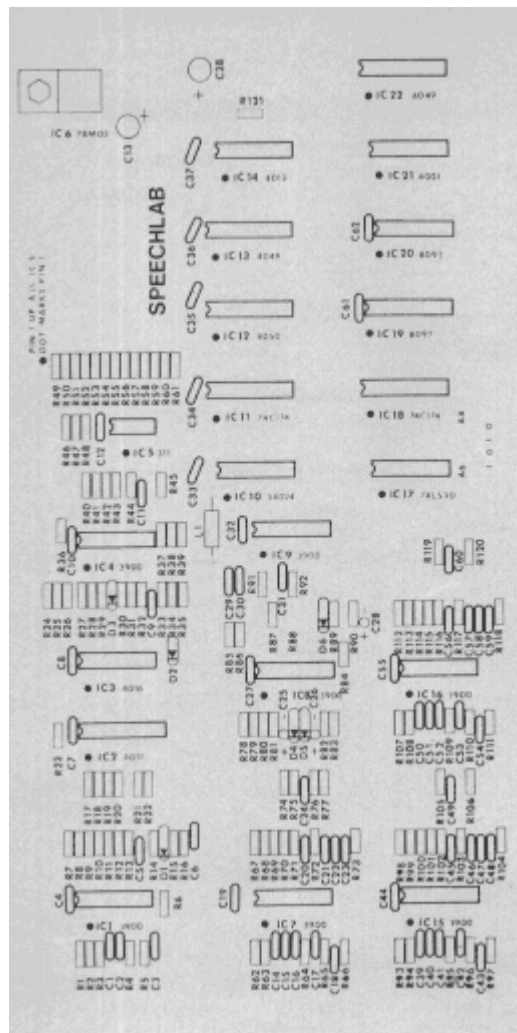


Fig. 9. Component layout for the Speechlab. See etching and drilling guide on previous page.

construction continued

All the components are mounted on one side of the board, with all the soldering done on the noncomponent side. Sockets are recommended for all IC's since most of them are MOS-types that may be damaged by improper handling. Integrated circuits IC1, IC4, IC7, IC8, IC9, IC15, and IC16 should be selected so they are capable of delivering a 4-volt output when using a 5-volt supply. Dual flipflop IC14 can be from any manufacturer but Fairchild, as their truth table is somewhat different from the conventional table.

Start construction by installing the voltage regulator (IC6), all the discrete components, and the IC sockets do not install the IC's at this time. Check the board for correct parts installation, and to make sure that there are no solder bridges between adjacent foil traces. Mount the board in an Altair bus connector, and check for the presence of 5 volts at the output of the voltage regulator and at appropriate socket pins. Remove the board from the computer.

Install IC2 through IC5, IC10 through IC14, and IC17 through IC22. Install the board back in the Altair bus connector, and turn on the computer. Load the test program of Table 1 at 100 (hex). NOTE: all program data in this article is in hex.

You must jump to your monitor routine at address 0164-0165. Load address 195 with 05 and run the program. This will input the fixed reference voltage levels to the A/D converter and check the signal paths from switch S1 to the computer data bus.

After running this program, examine locations 200 through 20F, 300 through 30F, and 400 through 40F. Location 200 through 20F should contain 12 approx. 4, 300 through 30F should contain 24 approx. 4, and 400 through 40F should contain 36 approx. 4.

Insert the remaining IC's in their sockets, load location 195 with 10, and run the test program (Table 1). This test uses the signal generator (G1) to create an input for the filters, amplifiers, and zero-crossing detector, and thereby checks the remaining signal paths on the board and calibrates the microphone preamplifier. After running the program, examine locations 200 to 20F to see if it contains 16 to 18. If not, adjust potentiometer R88 and rerun the program until these outputs occur.

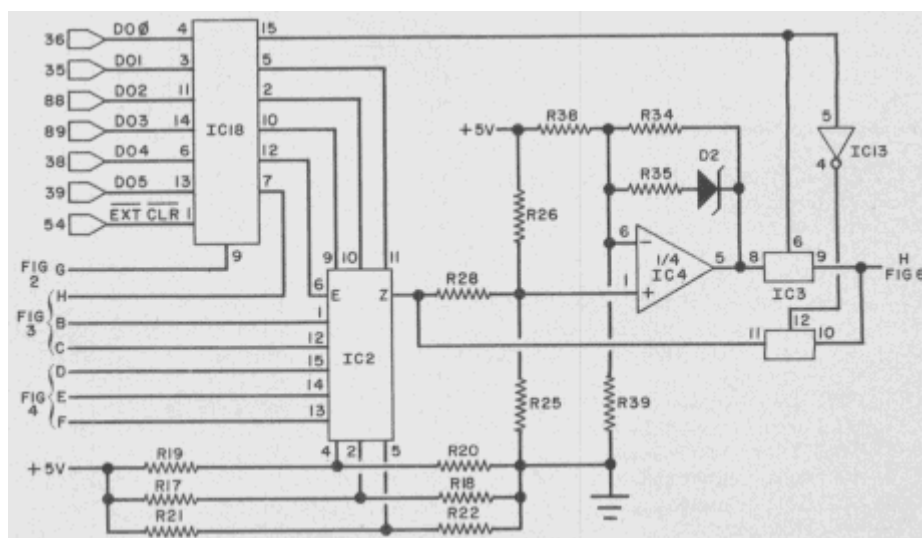


Fig. 5. Command latch (1C18) can activate tone generator and switch Si (1C2). Op amp (1/4 1C4) is logarithmic amplifier.


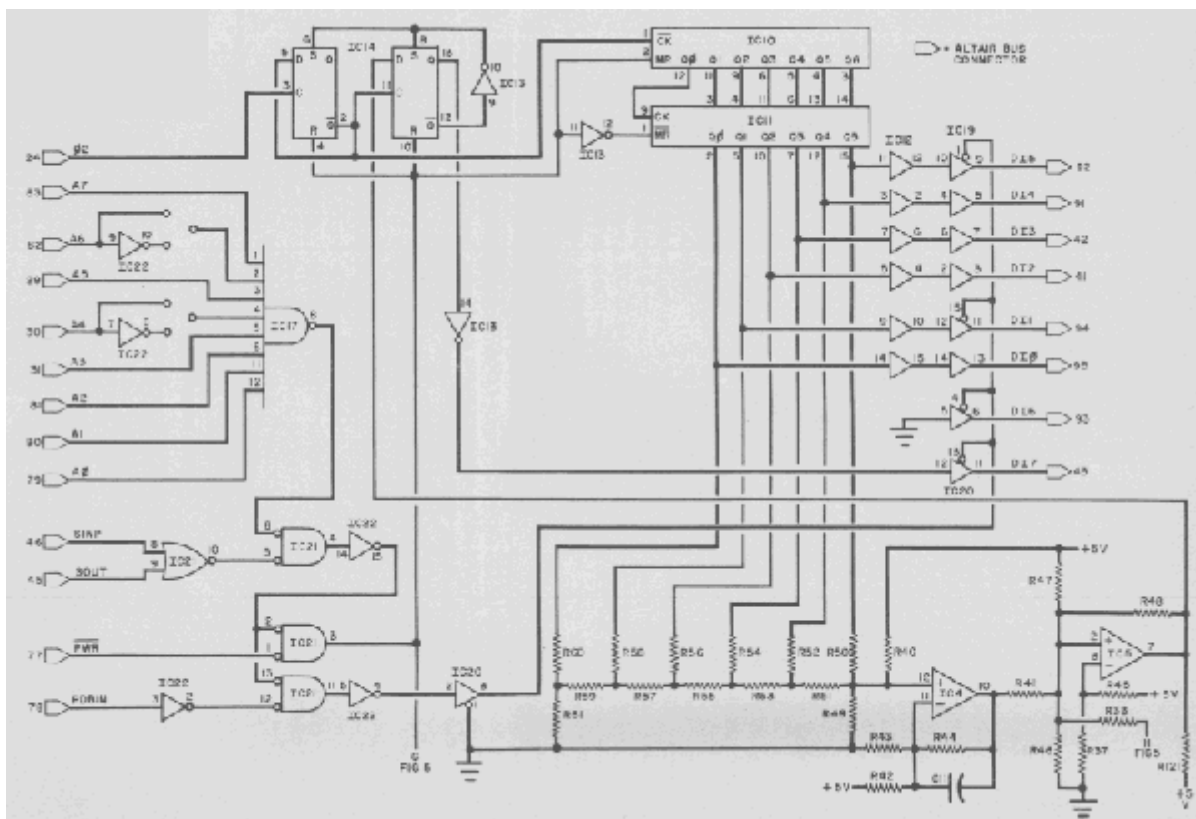


Fig. 6. IC17 circuit selects board address and IC14 forms S2. IC10 and IC11 form 6-bit A/D converter. Digitized data is then passed to computer.

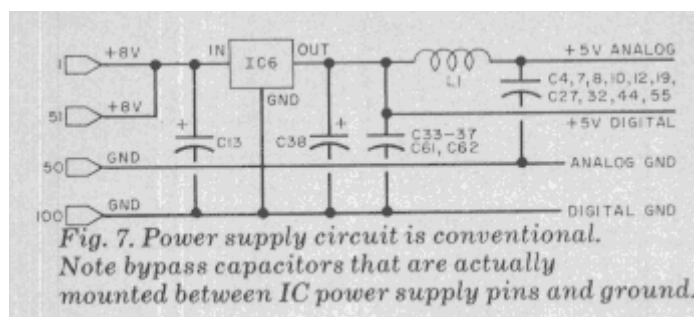

Calibration and Test Program.

The test program (**Table 1**) is a general purpose calibration, test, and diagnostic program for the SpeechLab. It loads at location 100 and requires memory from 100 to 600 for program and data areas. Locations 163-165 should be loaded with a lump to your monitor address so that the program will return control to your monitor after execution. If you do not have a monitor, place a halt at this location.

TABLE I

0100		ORG 100H
0100 =		START EQU 100H
0100 210002		LXI H,START+100H
0103 228D01		SHLD TEMP1
0106 210003		LXI H,START+200H
0109 228F01		SHLD TEMP2
010C 210004		LXI H,START+300H
010F 229101		SHLD TEMP3
0112 210005		LXI H,START+400H
0115 229301		SHLD TEMP4
0118 3A9501	GO	LDA COMAND
011B CD6601		CALL INPUT
011E 2A8D01		LHLD TEMP1
0121 77		MOV M,A
0122 2C		INR L
0123 228D01		SHLD TEMP1
0126 3A9501		LDA COMAND
0129 C601		ADI 1
012B CD6601		CALL INPUT
012E 2A8F01		LHLD TEMP2
0131 77		MOV M,A
0132 2C		INR L
0133 228F01		SHLD TEMP2
0136 3A9501		LDA COMAND
0139 C602		ADI 2
013B CD6601		CALL INPUT
013E 2A9301		LHLD TEMP3
0141 77		MOV M,A
0142 2C		INR L
0143 229101		SHLD TEMP3
0146 3A9501		LDA COMAND
0149 C603		ADI 3
014B CD6601		CALL INPUT
014E 2A9301		LHLD TEMP4
0151 77		MOV M,A
0152 2C		INR L
0153 229301		SHLD TEMP4
0156 CA5F01		JZ STOP
0159 CD7701		CALL DELAY
015C C31801		JMP GO
015F 3E00	STOP	MVI A,0
0161 D3AF		OUT OAFH
0163 C3XXXX		JMP SYSTEM
016A F620	INPUT	ORI 20H
016B D3AF		OUT OAFH
016A E6DF		ANI 0DFH
016C D3AF		OUT OAFH
016E D8AF	LOOP	IN OAFH
0170 17		RAL
0171 DA6E01		JC LOOP
0174 D8AF		IN OAFH
0176 C9		RET
0177 C5	DELAY	PUSH B
017B 3E05		MVI A,5
017A FED0	DELO	CPI 0
017C CABB01		JZ RETDEL
017F 0669		MVI B,69H
0181 00	DEL1	NOP
0182 00		NOP
0183 05		DCR B
0184 C2B101		JNZ DEL1
0187 3D		DCR A
0188 C37A01		JMP DELO
018B C1	RETDEL	POP B
018C C9		RET
C000 =		SYSTEM EQU C000H
018D		TEMP1 DS 2
018F		TEMP2 DS 2
0191		TEMP3 DS 2
0193		TEMP4 DS 2
0195 YY		COMAND EQU 5
0100 21 00 02 22 8D 01 21 00 03 22 8F 01 21 00 04 22		
0110 91 01 21 00 05 22 93 01 3A 95 01 CD 66 01 2A 8D		
0120 01 77 2C 22 8D 01 3A 95 01 C6 01 CD 66 01 2A 8F		
0130 01 77 2C 22 8F 01 3A 95 01 C6 02 CD 66 01 2A 91		
0140 01 77 2C 22 91 01 3A 95 01 C6 03 CD 66 01 2A 93		
0150 01 77 2C 22 93 01 CA 5F 01 CD 77 01 C3 1B 01 3E		
0160 00 D3 AF C3 53 00 FA 20 D3 AF E6 DF D3 AF D8 AF		
0170 17 DA 6E 01 D8 AF C9 C5 3E 05 FE 00 CA 8B 01 04		
0180 A9 00 00 05 C2 81 01 3D C3 7A 01 C1 C9 9B F7 F0		
0190 FE 57 DC 49 E2 AA		

Calibration and Test Program continued

The program collects four 256-byte buffers of data from four of the eight possible inputs to the A/D converter. The first of the four bands is specified by the Test Command word, which also specifies beeper on/off and linear or logarithmic scaling. The next three bands are 1, 2, and 3 greater than specified by the Test Command word. Each band is sampled every five milliseconds until 256 samples have been collected from each of the four bands. Data from the first band is stored in 200 to 2FF, the second band from 300 to 3FF, the third from 400 to 4FF, and the fourth from 500 to 5FF.

For example, if the Test Command word is set to 00, after the test program is run, the four data areas will contain numbers representing the outputs of band-0 (low frequency), band-1 (mid frequency), band-2 (high frequency), and band-3 (zerocrossing detector). Anything that was spoken into the microphone while the program was running, is filtered, converted into a binary number, and stored in the data areas.

If the Test Command word is set to 05, the first three data areas will contain constant numbers corresponding to the three reference voltage levels to the A/D converter on band 5, 6, and 7. This is useful for checking the A/D converter operation and isolating problem areas to one side or the other of the

8-to-1 analog switch S1. If the Test Command word is set to 10, signal generator G1 is enabled which begins to "beep" the microphone and connects the signalgenerator output into the microphone preamplifier A1. The four data areas contain data from bands 0, 1, 2, and 3 as when the Test Command word was 00, but the input signal comes from the signal generator rather than from the microphone. This allows calibration of the microphone preamplifier and isolates problems in one of the filter-averager chains.

Adding blt-3 to the command word will cause logarithmic rather than linear data scaling and will isolate problems to the log amplifier or either of the two analog switches comprising S2, the 2-to-1 analog switch.

Various combinations of bits in the Test Command word will allow quick calibration and fault isolation, and also provide a quick way to look at raw data from any input through the microphone.

Software.

A simple technique for speech recognition of the digits zero through nine with a recognition rate of 90% or better, is shown the flowchart of **Fig. 10** . An 8080 program for this algorithm is shown in **Table II** . The program starts at memory location 0100 and requires less than 4K bytes of storage including table space.

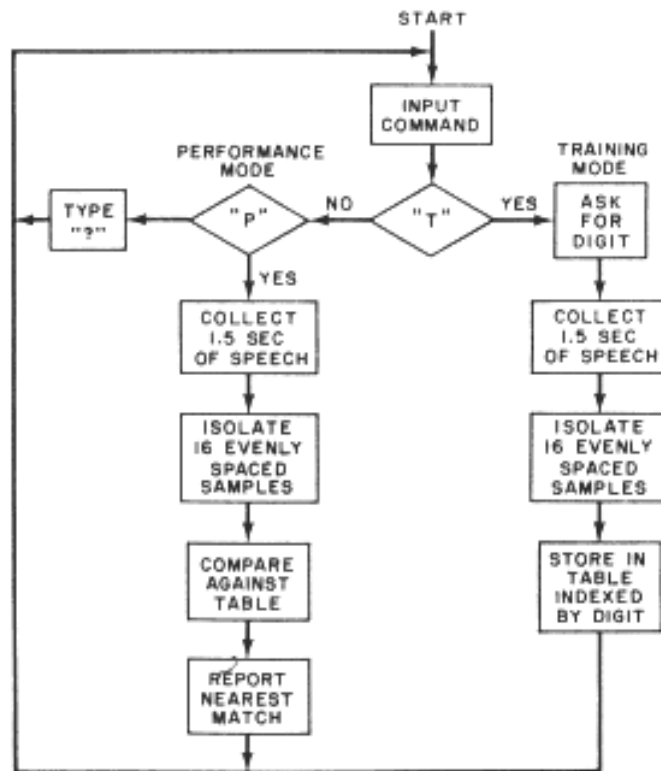


Fig. 10. Flow chart of a simple program that is used to "T" (train) and "P" (perform) a vocal operation. The program is shown in Table II

TABLE II

0100	11	00	10	CD	5B	03	21	35	0B	CD	3A	03	CD	0F	03	FE
0110	54	C2	1A	01	CD	33	01	C3	00	01	FE	50	C2	2B	01	CD
0120	5B	03	CD	79	01	CD	01	03	C3	00	01	3E	3F	CD	70	03
0130	C3	00	01	F5	C5	D5	E5	CD	5B	03	21	3D	0B	CD	3A	03
0140	CD	DA	03	32	6E	04	3C	47	3A	6D	04	B8	DA	2B	01	CD
0150	5B	03	CD	A3	02	CD	99	01	CD	07	94	3A	6E	04	4F	16
0160	40	CD	F7	02	11	13	07	CD	A3	03	60	69	0E	40	11	C8
0170	06	CD	0C	01	E1	01	C1	F1	C9	C5	D5	E5	CD	A3	02	CD
0180	99	01	CD	07	04	CD	3D	02	E1	D1	C1	C9	F5	E9	7E	23
0190	E9	77	23	0D	C2	0D	01	F1	C9	AE	00	21	6F	04	CD	F9
01A0	03	FE	06	D2	E2	01	79	FE	96	C2	9E	01	21	44	0B	C3
01B0	9D	02	79	3D	32	0B	07	47	CD	F5	0E	01	FE	0A	CC	01
01C0	79	FE	96	C2	0B	01	21	4E	0B	C3	9D	02	79	3D	3D	32
01D0	09	07	90	3C	32	C7	E6	FE	0A	DA	A6	01	0E	03	CD	F9
01E0	03	FE	06	D2	ED	01	79	FE	0A	C2	DE	01	C9	3A	C7	06
01F0	01	4F	3A	08	07	01	4F	C3	0B	01	21	FF	FF	22	13	0B
0200	3E	00	32	6E	04	3A	6D	04	3D	4F	06	02	C5	79	07	4F
0210	21	15	0B	09	46	23	4E	21	13	0B	56	23	5E	CD	02	03
0220	DA	2B	02	C1	0D	FA	39	02	C3	0C	02	21	13	0B	70	23
0230	71	C1	79	32	6E	04	C3	24	02	3A	6E	04	C9	CD	64	02
0240	06	00	48	16	48	3E	0E	5F	21	13	07	CD	D5	03	CD	75
0250	02	1C	7B	FE	3F	C2	48	02	04	3A	6D	04	B8	C2	42	02
0260	CD	FA	01	C9	3A	6D	04	07	4F	3E	00	21	15	0B	77	23
0270	0D	C2	6E	02	C9	E5	D5	C5	F5	21	C8	06	16	00	19	96
0280	F2	05	02	2F	3C	57	7B	07	21	15	0B	4F	06	00	09	23
0290	7A	06	77	D2	98	02	2B	34	F1	C1	D1	E1	C9	CD	3A	03
02A0	C3	00	01	3E	FA	CD	E3	02	CD	40	03	3E	64	CD	E3	02
02B0	21	6F	04	1E	96	16	08	7A	FE	04	CA	C6	02	CD	D3	02
02C0	77	23	14	C3	B7	02	3E	0A	CD	E3	02	1D	C2	05	02	CD
02D0	4B	03	C9	F6	20	D3	AF	E6	DF	D3	AF	DB	AF	17	DA	0B
02E0	02	1F	C9	C5	FE	00	CA	F5	02	06	69	00	00	05	C2	EB
02F0	02	3D	C3	E4	02	C1	C9	F5	D5	06	00	1E	09	79	1F	4F
0300	1D	CA	0E	03	78	02	09	03	02	1F	47	C3	FD	02	D1	F1
0310	C9	F5	D5	1E	09	70	47	79	17	4F	1D	CA	2F	03	70	17
0320	D2	27	03	92	C3	16	03	92	D2	16	03	02	C3	16	03	17
0330	5F	3E	FF	A9	4F	7B	1F	D1	F1	C9	7E	FE	00	CA	47	03
0340	CD	70	03	21	C3	03	CD	0B	03	C9	F5	3E	10	D3	AF	
0350	3E	64	CD	E3	02	3E	00	D3	AF	F1	C9	F5	3E	0D	CD	70
0360	03	3E	0A	CD	70	03	3E	00	CD	70	03	CD	70	03	F1	C9
0370	F5	DB	00	07	D2	71	03	F1	03	01	C9	00	00	00	00	00
0380	00	E6	0F	C6	30	FE	3A	DA	70	03	C6	07	C3	70	03	DB
0390	00	E6	40	CA	0F	03	DB	01	E6	7F	C3	70	03	00	00	00
03A0	00	00	00	E9	09	08	42	40	C9	F5	79	93	4F	78	9A	47
03B0	F1	C9	32	0A	07	78	0A	CA	BE	03	3A	0A	07	C9	79	0B
03C0	3A	0A	07	C9	F5	C5	D5	CD	F7	02	09	05	6F	D2	D1	03
03D0	24	D1	C1	F1	C9	CD	C4	03	7E	C9	CD	0F	03	E6	7F	FE
03E0	30	DA	2B	01	FE	3A	DA	P6	03	FE	41	DA	2B	01	FE	47
03F0	3F	DA	2B	01	D6	07	D6	30	C9	AF	C5	06	03	05	23	05
0400	C2	FD	03	C1	23	0C	C9	21	C8	06	22	0B	07	3A	C7	06
0410	4F	16	0A	CD	07	02	16	10	CD	11	03	26	00	69	22	11
0420	07	21	00	00	22	0F	07	1E	10	D5	2A	0F	07	44	4D	16
0430	0A	CD	11	03	06	00	3A	0B	07	5F	16	00	CD	A3	03	16
0440	04	CD	F7	02	21	6F	04	09	54	5D	2A	0B	07	0E	04	CD
0450	0C	01	22	0B	07	2A	0F	07	44	4D	2A	11	07	54	5D	CD
0460	A3	03	60	69	22	0F	07	D1	1D	C2	29	04	C9	10	CD	EF
0B30	DA	0C	FE	02	C2	54	20	4F	52	20	50	3F	00	4E	55	4D
0B40	42	45	52	00	4E	4F	20	53	50	45	45	43	48	00	4F	55
0B50	54	20	4F	46	20	57	49	4E	44	4F	57	00	00	32	5C	00

Software continued


There are two modes of operation training and performance. During training, speech examples of the digits are read into the microphone and the parameters of the speech input are extracted and placed in the tables. In the performance mode, an unknown utterance is presented and recognized. To use the program, enter it into the computer starting at location 0100, and then run the program. The Teletype will respond with "T" (train) or "P" (perform). Type a "T" and the Teletype will respond with "NUMBER?" which can be between 0 and F. Type the digit you desire, and the microphone will emit a "beep" indicating that the speech window is open. When this beep occurs, vocalize the same digit you just typed in. The microphone will beep again to indicate that the speech window is now closed. The machine will then type T or P again. You answer with a T, and the process is continued as long as you want. Do not exceed 16 entries with this sample program.

Once you have some vocalized digits in memory, run the program again. This time, when the Teletype asks T or P, answer with a P (for perform). Now, as you speak the digits into the microphone, the Teletype will respond by typing that digit. When used in a quiet room, with the same vocalization, this algorithm can be expected to have a recognition rate greater than 90%.

The program works as follows: the sampling subroutine is entered to obtain a sample of the amplitude every 10 milliseconds in each of the three frequency bands and to estimate the number of zero crossings during each time period. One hundred and fifty samples are collected, allowing up to 1.5 seconds of speech (between microphone "beeps"). A preset threshold is used to find the beginning and end of the word. The duration of the word can now be computed by a simple subtraction. Typically, this duration will be about 400-milliseconds for the digits. The duration time is divided by 16 to select 16

evenly spaced parameters from the three bands and zero crossing information.

The 64 bytes obtained (16 parameters from each of the four bands) are compared with similar parameters which were collected during the training mode. A summation (running total) of the difference between the 64 parameters of the sample and the parameters of the training "templates" is computed. The totals represent a measure of the difference between the sample and each of the previously stored templates. The template with the smallest difference from the sample is then selected as the answer (output). The above algorithm, while relatively simple, illustrates many of the basic concepts of speech recognition. A manual supplied with the Speechlab kit contains descriptions of other approaches to speech recognition, along with sample programs to demonstrate the techniques of speech recognition.

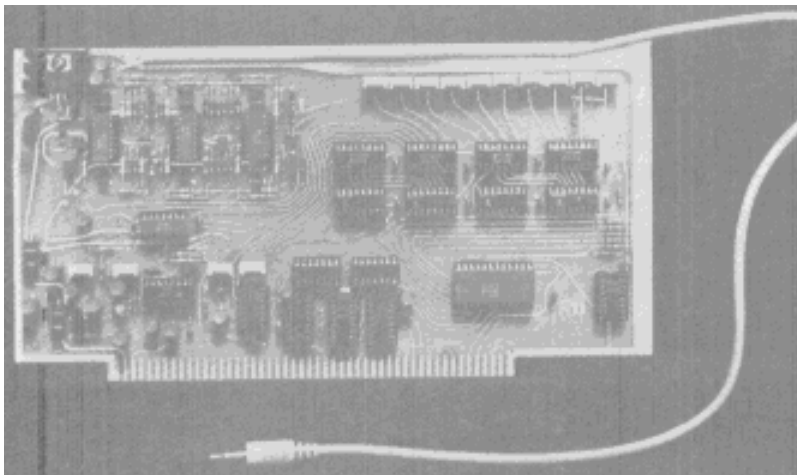

BY LESLIE SOLOMON, Technical Editor

While testing the speechlab, we borrowed an AI Cybernetic Systems (Box 4691, University Park, NM 88003) Model1000 Speech Synthesizer (\$325, assembled) to see if our microcomputer could "talk" as well as "hear." The Model 1000 is designed to fit into one slot of an Allair bus and delivers its output via an audio cable that can be plugged into any audio amplifier system. The output level is 0.6 volt p-p; impedance is 1000 ohms; and frequency range is 150 to 4500 Hz. This synthesizer is phoneme-oriented. Accordingly, you can program it to say anything, as opposed to speech synthesizers that have only several words fixed in ROM. Essentially, the Model 1000 is a hardwired analog of the human vocal tract and various portions of the circuit emulate the vocal cords, the lungs, and the variable-frequency resonant acoustic cavity of the mouth, tongue, lips and teeth.

All the information necessary to perform the synthesis functions are located within a ROM that is accessed by the program. Words and sentences are formed by supplying a string of ASCII characters as would be done when outputting to any port, except that these strings also use some non-alphanumeric characters (i.e., the "+" is used to form "th" as in "thaw" or "earth"). Each ASCII character represents a particular phonetic sound or phoneme. If desired, you can create a program that produces simultaneous printout and "voiceout" of the same string.

The device requires very little software to implement: less than 50 bytes of assembly language or a handful of BASIC statements. The manual accompanying the synthesizer covers speech generation in detail, how it is created, and what is involved. It also illustrates how to "mechanize" speech, with several examples shown.

After working with the synthesizer for a couple of weeks, we found that we have a lot to learn about how humans create speech. After many hours of studying, experimenting, and redoing programs, we made the Model-1000 utter some recognizable sentences. It is not easy, our experience showed, even when one uses the wealth of instructions provided.

Working with a phoneme-oriented speech synthesizer is a little like learning to use a microprocessor. All the logic is there, but programming it properly is another story. Like working with a processor for the first time, one must crawl frustratingly before walking. Slowly, however, the ideas start to percolate. Our computer still talks with a rather heavy "robotic" accent, but we have hopes that someday it will "humanize". To paraphrase Sam Johnson: "Sir, a computer talking is like a dog walking on its hind legs. It is not done well; but you are surprised to find it done at all." We have a long road ahead to the "HAL-9000", but the first step has been taken.

Popular Electronics may 1977